


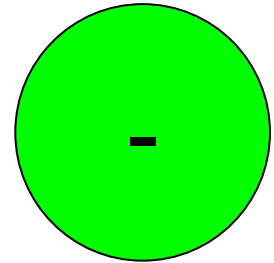


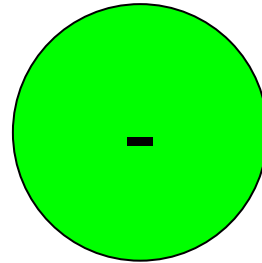

Introduction to Electronics

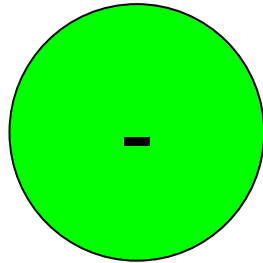

Circuits and Electricity

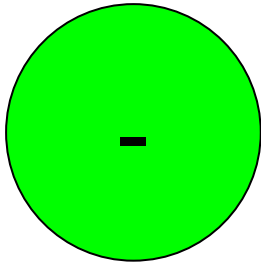



Ohm's Law or Your New Best Friend

$$V = IR$$


Voltage Current Resistance

Diagram illustrating Ohm's Law: $V = IR$. The variables are labeled below the equation with arrows pointing to them: Voltage points to V , Current points to I , and Resistance points to R .




Resistance

Resistance

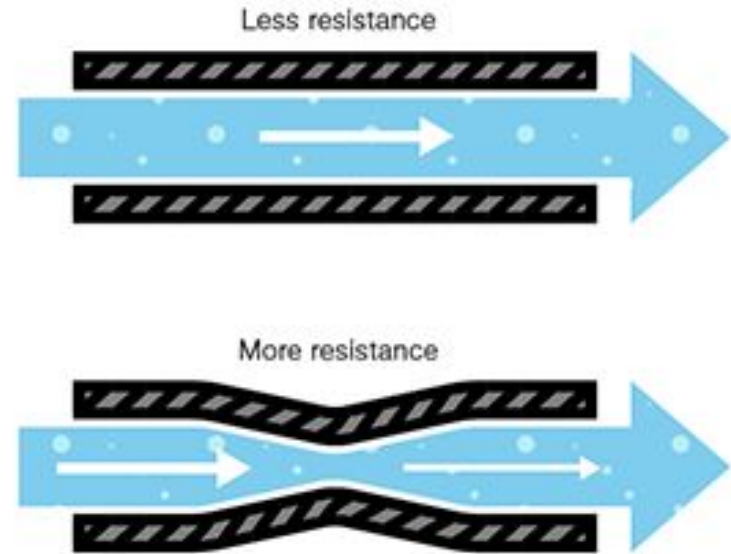




Resistor

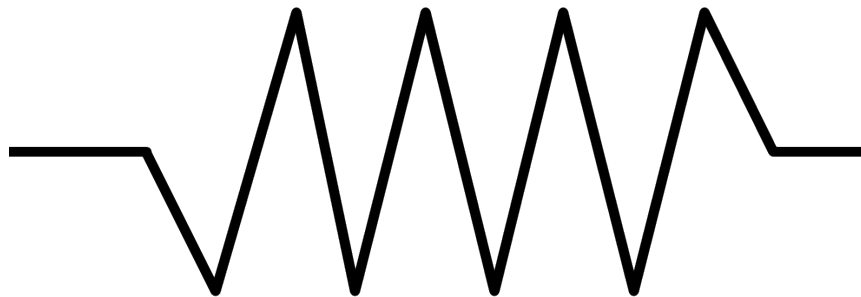




Diode

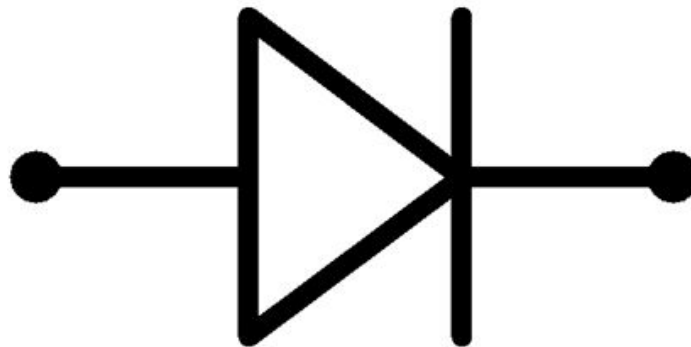




LED

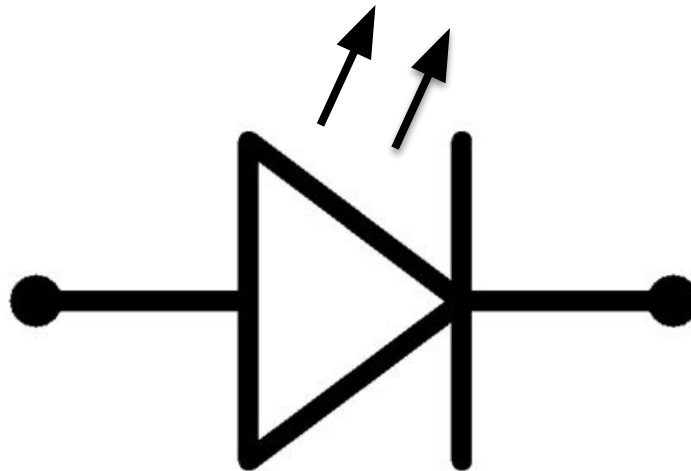



Breadboards

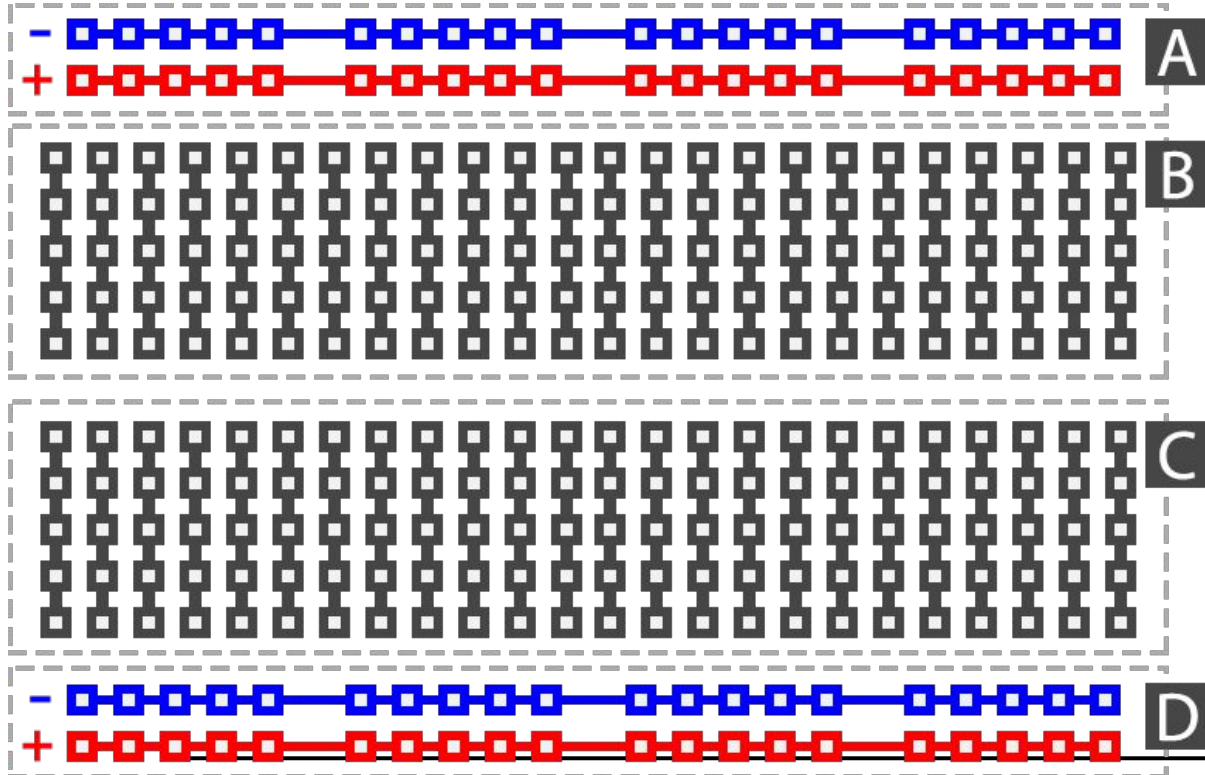



Circuit 1 - LED and resistor circuit

You will need:

- 1x 9V battery
- 1x battery clip
- 1x breadboard
- 1x 470ohm resistor
- 1x LED of any color
- jumper wires




+9V



470



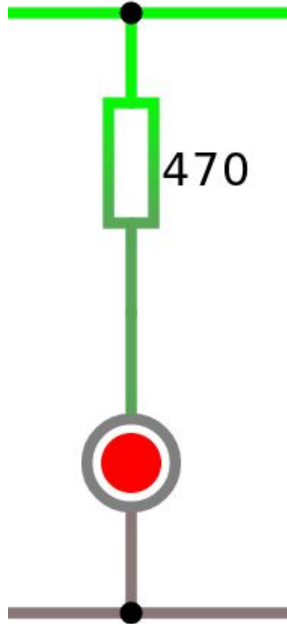

9V across whole thing

2V across LED

$9 - 2 = 7\text{V}$ across resistor

$$V = IR$$


$$V = 7 \quad I = 15\text{mA}$$

$$R = 466.6666666\dots$$

Standard series of resistors

... 330, 390, 470, 560, 680...

Choose next one up

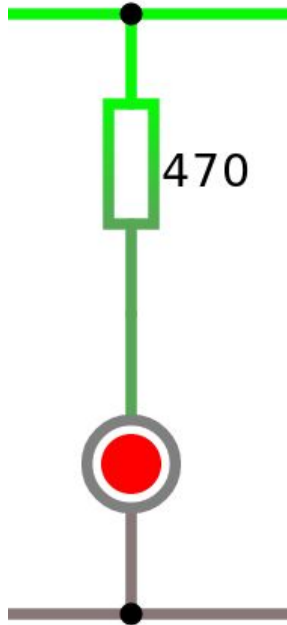

9V across whole thing

2V across LED

$9 - 2 = 7\text{V}$ across resistor

$$V = IR$$


$$V = 7 \quad I = 15\text{mA}$$

$$R = 466.6666666\dots$$

Standard series of resistors

... 330, 390, 470, 560, 680...

Choose next one up

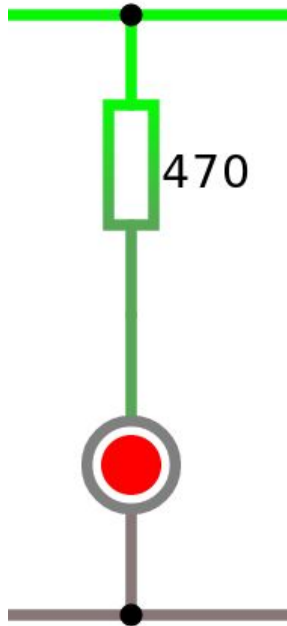

9V across whole thing

2V across LED

$9 - 2 = 7\text{V}$ across resistor

$V = IR$



$V = 7$ $I = 15\text{mA}$

$R = 466.6666666\dots$

Standard series of resistors

... 330, 390, 470, 560, 680...

Choose next one up

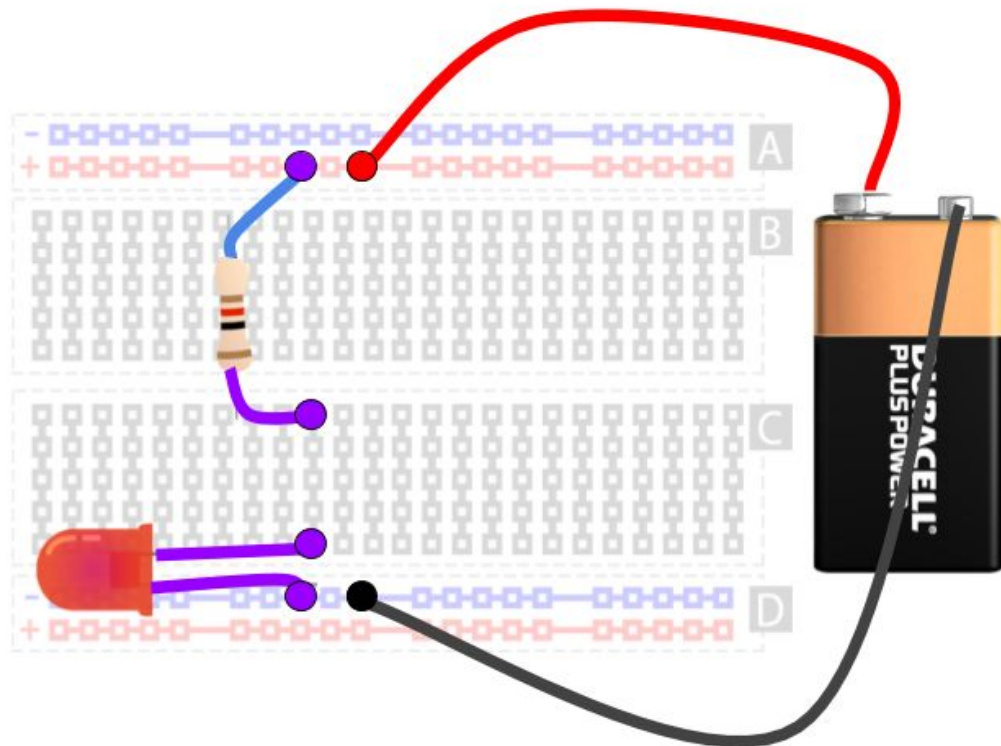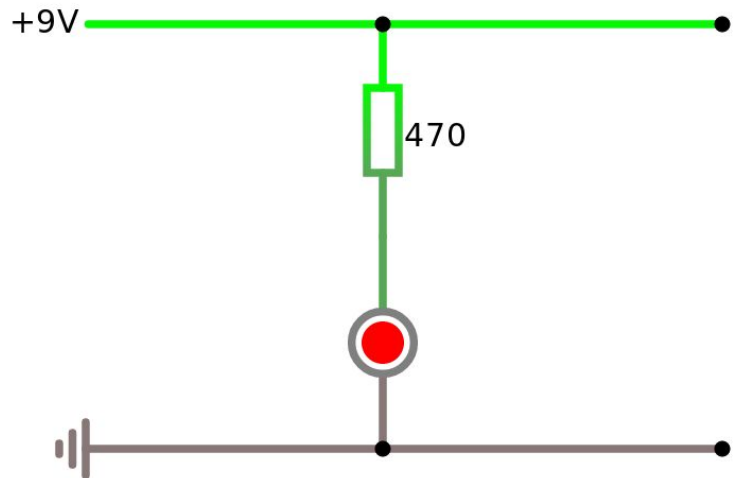



+9V





470






Transistors (NPN and PNP)

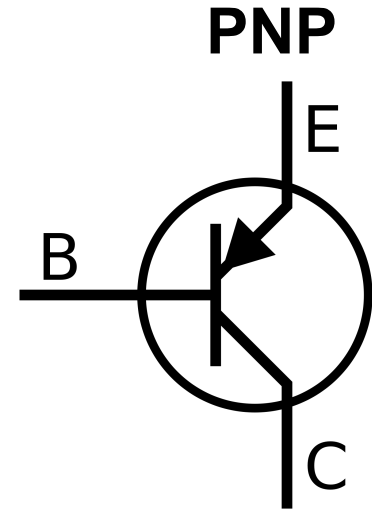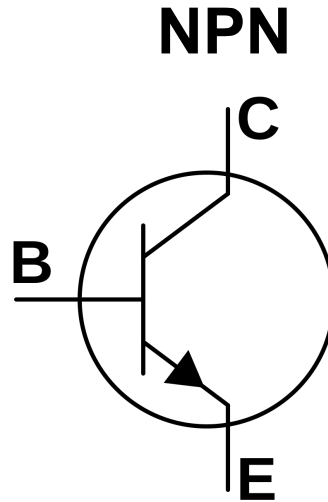




Circuit 2 - Touch Sensor

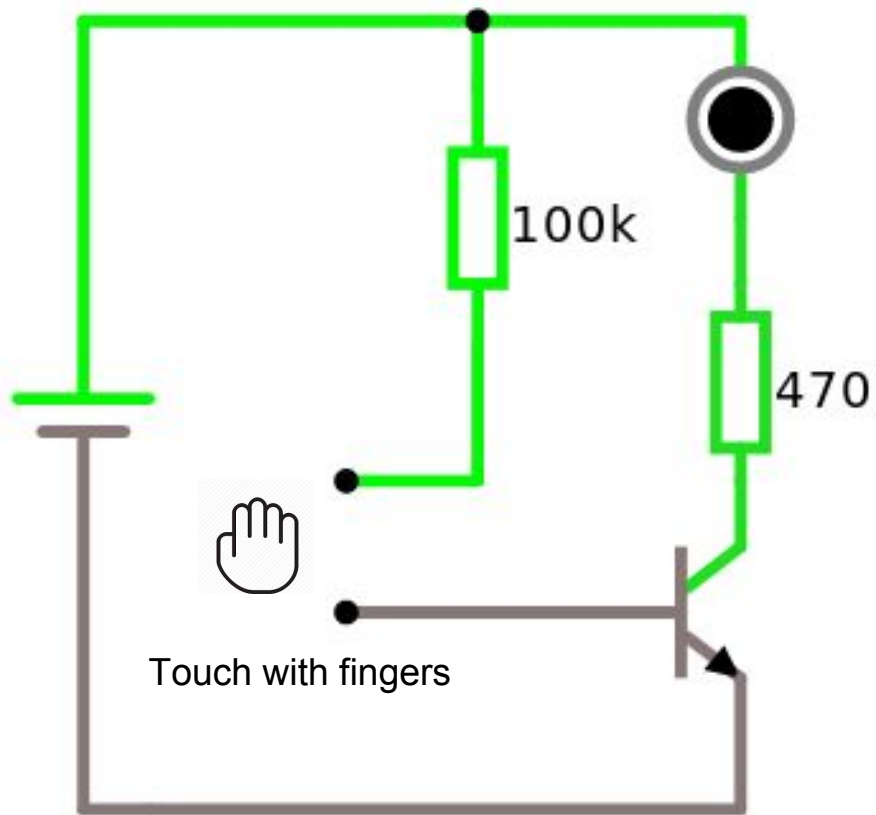- 1x 9V battery
 - 1x battery clip
 - 1x breadboard
 - 1x NPN transistor
 - 1x 470 ohm resistor
 - 1x 100 kohm resistor
 - 1x LED of any color
 - jumper wires
-







Potential dividers

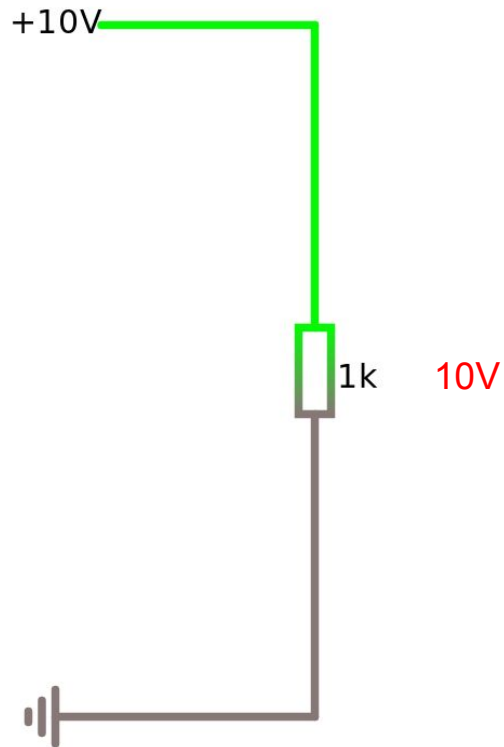






Potential dividers

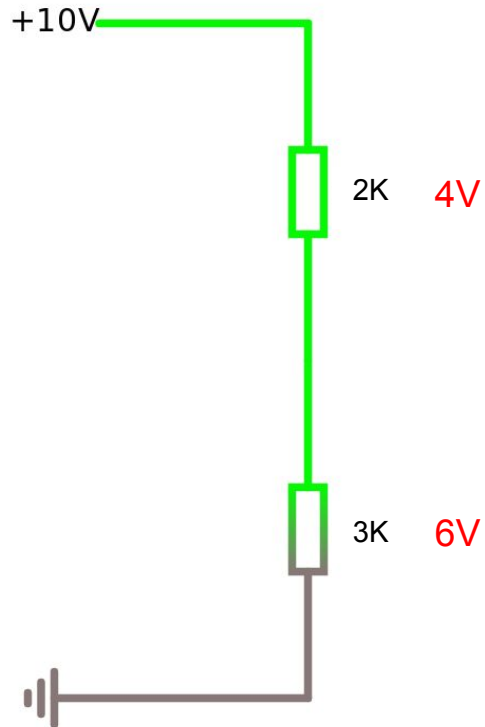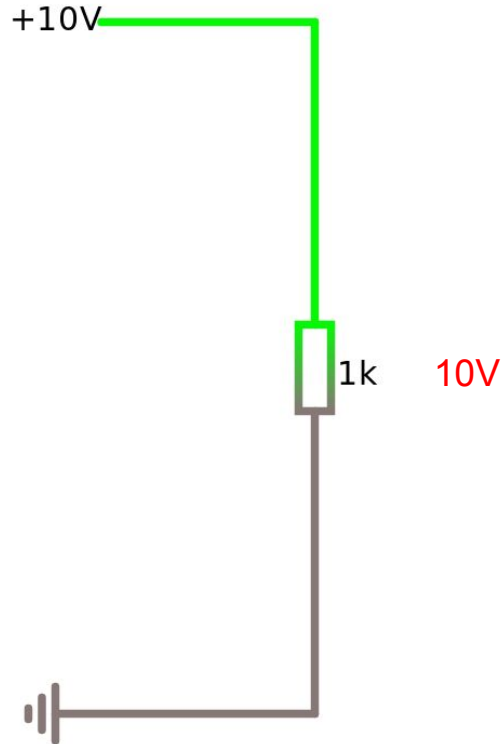




Potential dividers

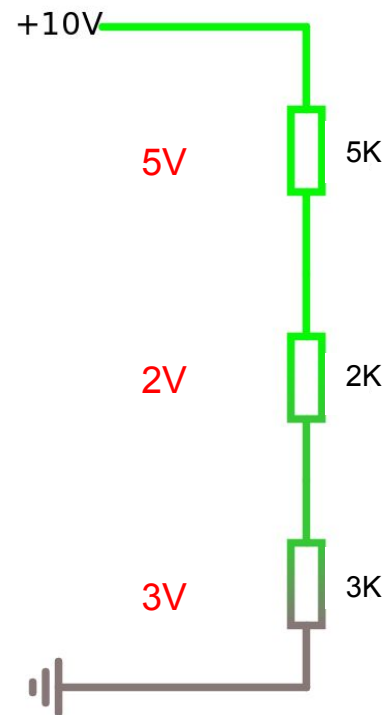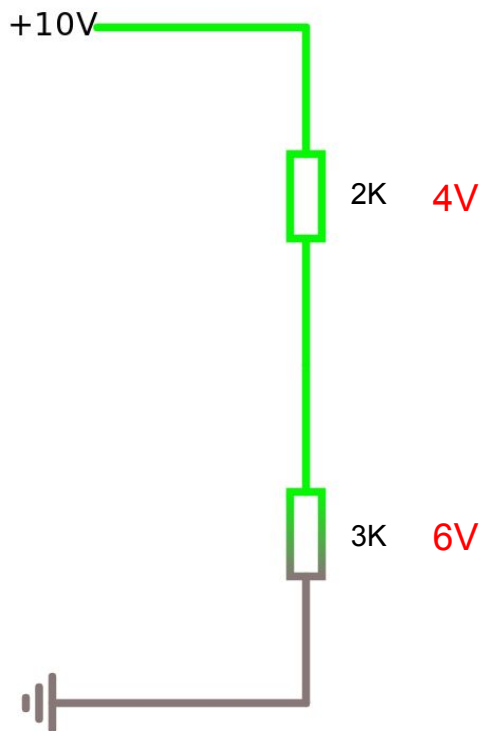
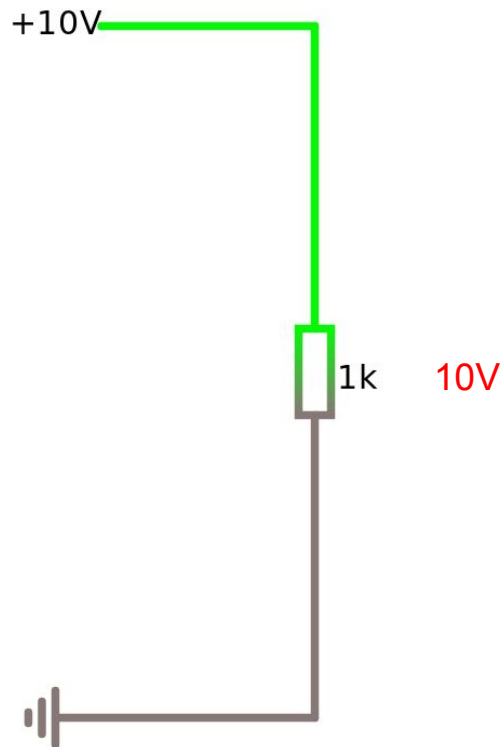




Circuit 4 - LDR



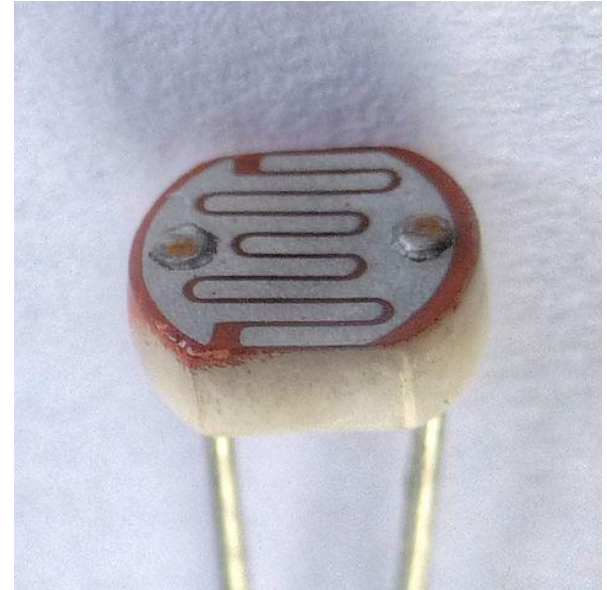
- 1x 9V battery
- 1x battery clip
- 1x breadboard
- 1x 470 ohm resistor
- 1x 100 kohm resistor
- 1x LDR
- 1x LED
- 1x NPN transistor
- jumper wires



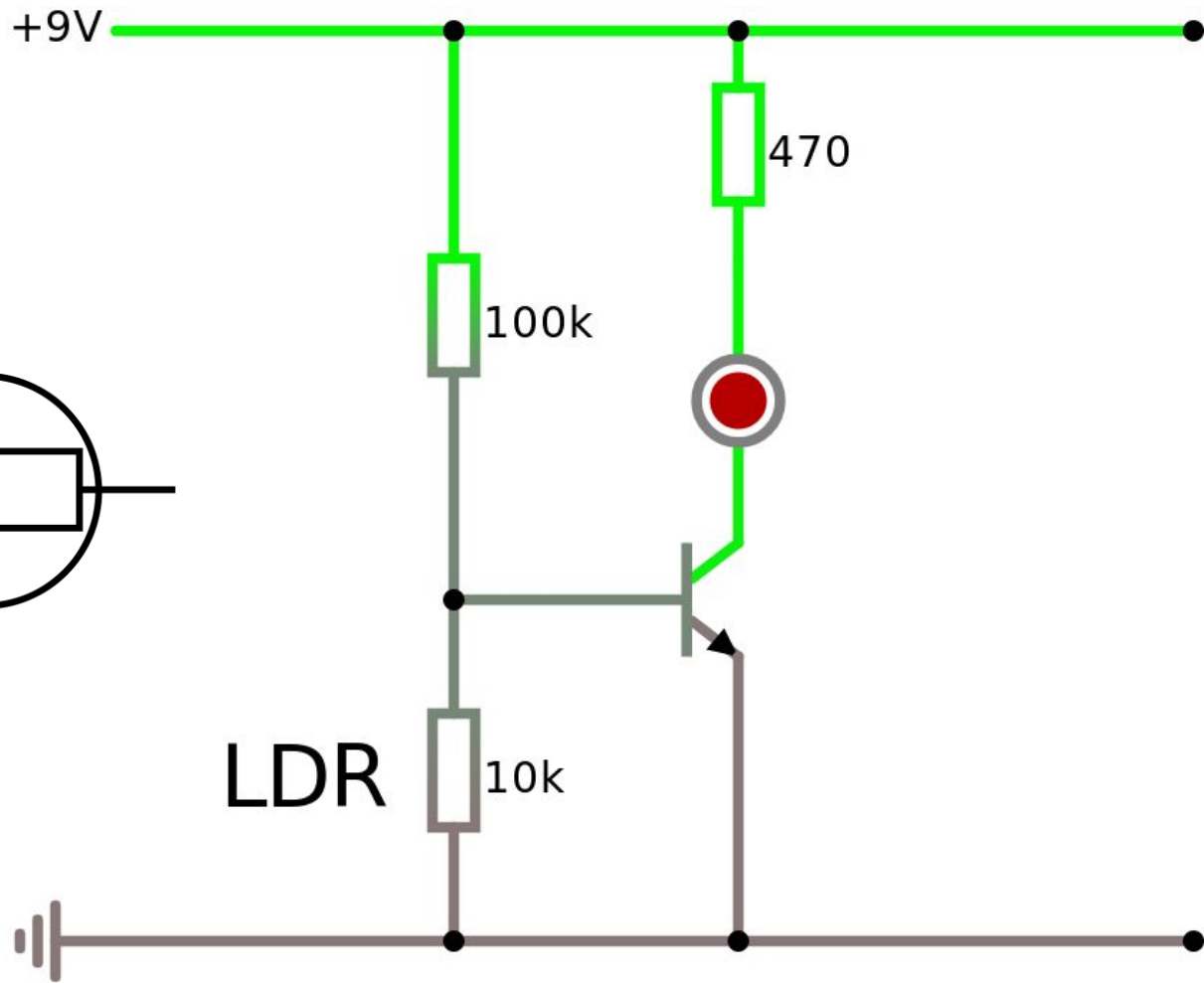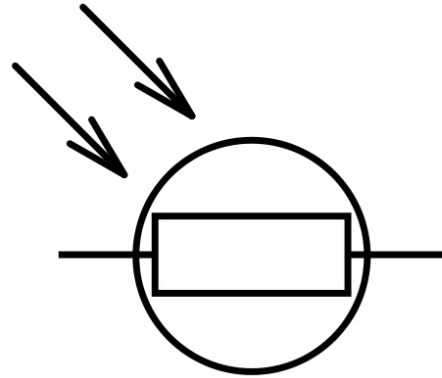




Capacitor

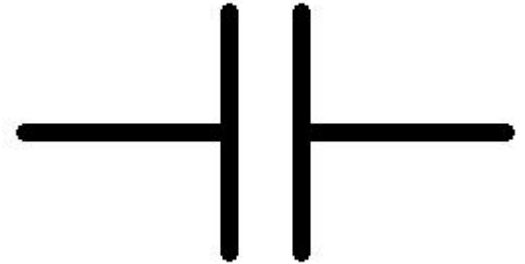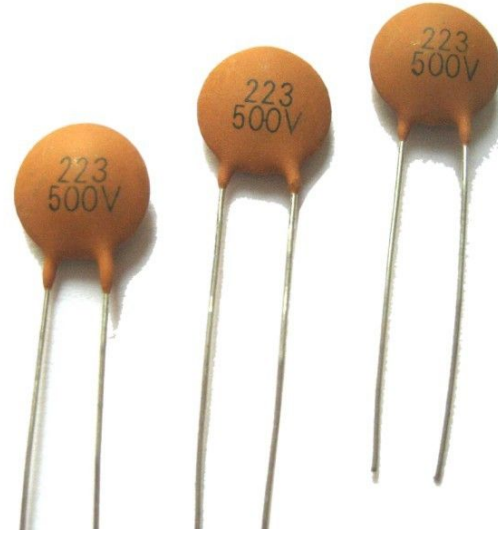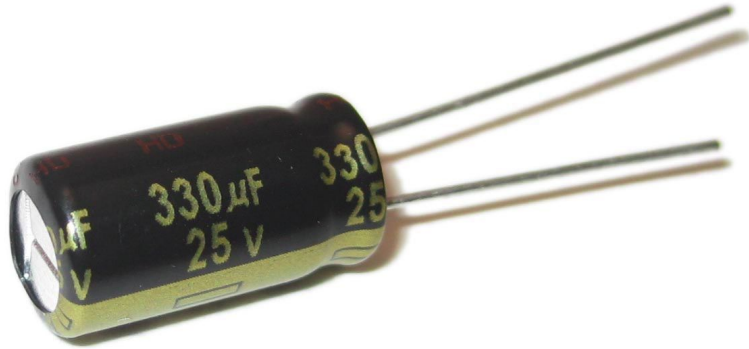



Circuit 5 - Capacitor demonstration

- 1x 9V battery
 - 1x battery clip
 - 1x breadboard
 - 1x 470 ohm resistor
 - 1x 100 uF capacitor
 - 1x NPN transistor
 - 1x LED of any color
 - jumper wires
-

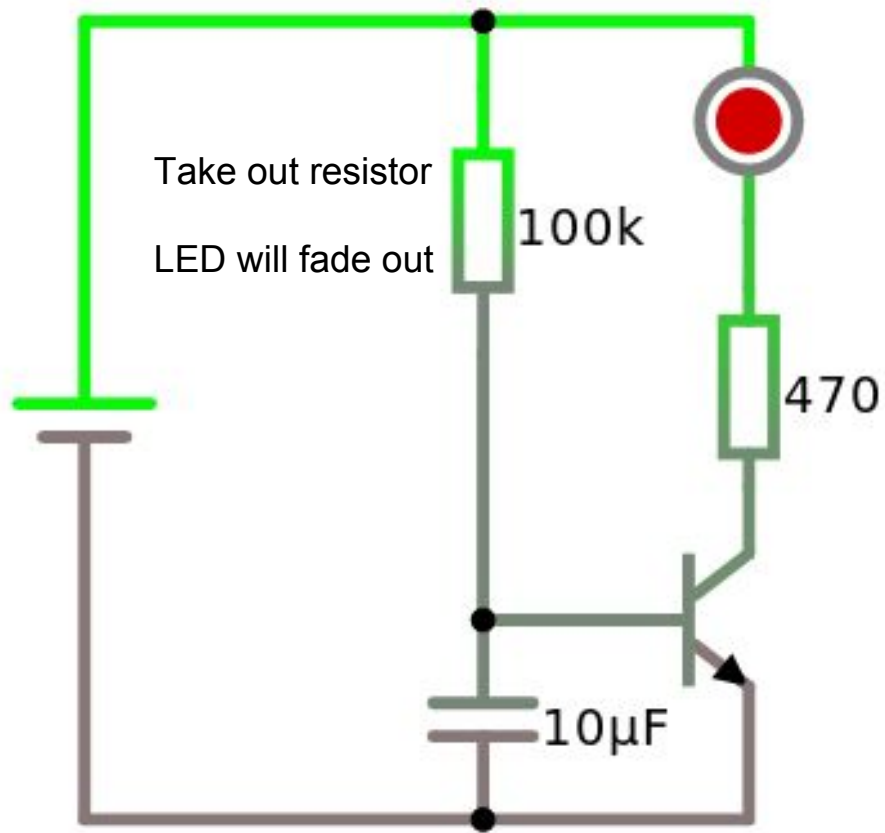



Circuit 6 - blinking LED's

- 1x 9V battery
 - 1x battery clip
 - 1x breadboard
 - 2x 1k ohm resistor
 - 2x 100 kohm resistor
 - 2x NPN transistor
 - 2x 10uF capacitor
 - 2x LED of any color
 - jumper wires
-

